

[Total No. of Question -02]

[Total No. of Pages - 01]

G H Raison
College

G H Raison College of Engineering and Management, Pune

(An Empowered Autonomous Institute affiliated to Savitribai Phule, Pune University, NAAC Accredited "A+" Grade)

First Year B. Tech.

CAE I / Term II / AY 2025-26 (2023 Pattern)

Digital Logic Design (23UESL1105)

(Time: - 01 Hour)

(Max. Marks : 20)

Instructions to the students:

- i) All questions are compulsory.
- ii) Calculator is allowed
- iii) Figures to the right indicate full marks.

Question No		Marks	CO	BL
Q.1 a)	Convert the following Decimal number to Hexadecimal number (445.27) ₁₀ (122.75) ₁₀	5	CO1	L2
OR				
Q.1 b)	What is Excess -3 code? Convert the decimal number (48) ₁₀ into Excess-3 code. Convert binary number (110101) ₂ to gray code.	5	CO1	L2
Q.1 c)	Reduce the following equation using Boolean Algebra theorems, and implement using logic gates. $F(A,B,C) = A'BC + A'B' + A'B'C'$	5	CO1	L2
OR				
Q.1 d)	Perform the subtraction on following number using 1's compliment technique 1. (23 - 13) ₁₀ 2. (15 - 25) ₁₀	5	CO1	L2
Q.2 a)	What is flip-flop? How to design T FF from JK FF? Also write the application of T FF.	5	CO2	L2
OR				
Q.2 b)	Convert the following function into standard POS form $F(A,B,C) = (B + C)(A' + B')(A' + C')$	5	CO2	L2
Q.2 c)	What is Multiplexer? Design 8:1 multiplexer using truth table and circuit diagram using logic gates.	5	CO2	L2
OR				
Q.2 d)	Design Half Adder circuit. Draw logic diagram and truth table.	5	CO2	L2

BL - Bloom's Taxonomy Levels (1- Remember, 2- Understand, 3 - Apply, 4 - Analyze, 5 - Evaluate 6 - Create)